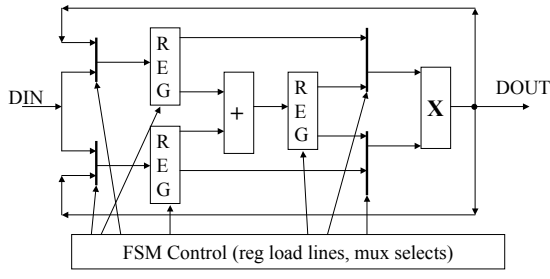


Finite State Machines

- The job of a finite state machine is to sequence operations on a datapath



BR 1/99

1

Algorithmic State Chart (ASM)

- An ASM chart can be used to describe FSM behavior


Only three action signals can appear within an ASM chart:

- State box** (rectangle): Each box represents a state. Outputs within a state box is an UNCONDITIONAL output (always asserted in this state).
- Decision box** (diamond): A condition in this box will decide next state condition.
- Conditional output box** (oval): If present, will always follow a decision box; output within it is conditional.

BR 1/99


2

Example ASM Chart

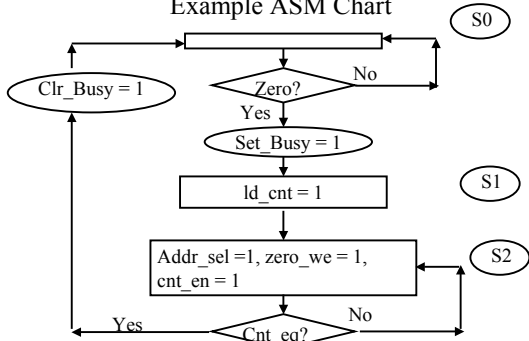

BR 1/99

3

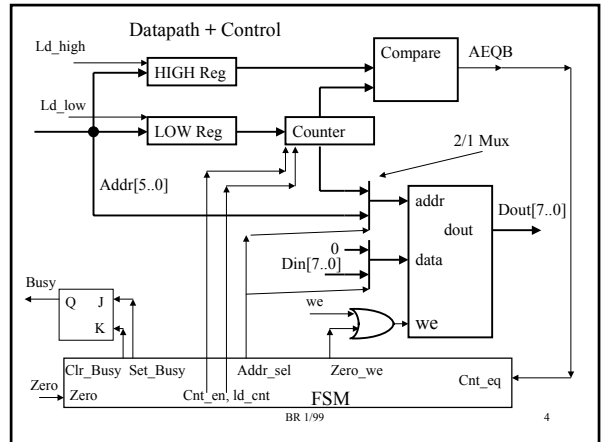

BR 1/99

4

Comments about ASM Example

- How many states?
 - Three states, count the boxes
- How many inputs?
 - Two inputs (Zero, Cnt_eq). Count signals within decision boxes. Inputs ALWAYS appear within decision boxes.
- How many outputs?
 - 4 unconditional outputs (count signals within state boxes)
 - 2 conditional output (count signals within conditional output boxes)
 - Outputs ALWAYS appear in either state boxes or conditional output boxes.


BR 1/99

5

FSM Implementation

Will always use VHDL to implement FSMs in this class.

 Most common method is to use ONE process for implementing state registers, ONE process for implementing logic.



BR 1/99

6

State Encoding

- How we encode the states is an implementation decision
- For K states, need a minimum of $\log_2(K)$ Dffs.
- Minimal encoding for example is two FFs
 - S0 = 00, S1 = 01, S2 = 10 (counting order)
 - S0 = 00, S1 = 01, S2 = 11, (Gray code for S0->S1->S2)
Gray code usually faster, less logic than counting order
- One Hot encoding, one FF per state
 - S0 = 001, S1 = 010, S2 = 100
 - For large FSMs (> 16 states), one hot can be faster than minimal encoding

BR 1/99

7

FSM Entity Declaration, Part of Architecture

```
library ieee;
use ieee.std_logic_1164.all;

-- FSM entity for RAM Zero example
entity ramfsm is
port ( clk, reset: in std_logic;
      zero, cnt_eq: in std_logic; -- control inputs
      set_busy, clr_busy: out std_logic; -- control outputs
      addr_sel, cnt_en, ld_cnt, zero_we: out std_logic;
      state: out std_logic_vector(1 downto 0) -- state out for debugging
);

end ramfsm;

architecture a of ramfsm is
signal pstate: std_logic_vector(1 downto 0);
CONSTANT S0 : std_logic_vector(1 downto 0) := "00"; --- state encoding
CONSTANT S1 : std_logic_vector(1 downto 0) := "01";
CONSTANT S2 : std_logic_vector(1 downto 0) := "10";
BR 1/99
```

8

FSM Architecture, One process (cont)

```
begin
state <= pstate; -- look at present state for debugging purposes
stateff:process(clk) -- process has state transitions ONLY
begin
if (reset = '1') then pstate <= S0;
elsif (clk'event and clk='1') then -- rising edge of clock
CASE pstate IS
WHEN S0 => if (zero = '1') then pstate <= S1; end if;
WHEN S1 => pstate <= S2;
WHEN S2 => if (cnt_eq = '1') then pstate <= S0; end if;
WHEN others => pstate <= S0;
end case;
end if;
end process stateff;

set_busy <= '1' when (pstate = S0 and zero = '1') else '0';
ld_cnt <= '1' when (pstate = S1) else '0';
addr_sel <= '1' when (pstate = S2) else '0';
zero_we <= '1' when (pstate = S2) else '0';
cnt_en <= '1' when (pstate = S2) else '0';
clr_busy <= '1' when (pstate = S2 and cnt_eq = '1') else '0';
end a;
```

BR 1/99

9

Comments on One Process Implementation

- *Stateff* process defines state FFs and transitions between states
- Outputs of FSM are separate concurrent statements outside of process
- Can be confusing since you separate out the FSM outputs from their state definitions within the CASE statement
- If output code is placed within CASE statement then they would be protected by the clock check and thus would have DFFs placed on their outputs
 - 1 clock cycle of latency to output assertion

BR 1/99

10

FSM Architecture, Two processes

```
architecture a of ramfsm is
signal pstate, nstate: std_logic_vector(1 downto 0);

CONSTANT S0 : std_logic_vector(1 downto 0) := "00"; --- state encoding
CONSTANT S1 : std_logic_vector(1 downto 0) := "01";
CONSTANT S2 : std_logic_vector(1 downto 0) := "10";

begin
state <= pstate; -- look at present state for debugging purposes

stateff:process(clk) -- process has DFFs only
begin
if (reset = '1') then pstate <= S0;
elsif (clk'event and clk='1') then
pstate <= nstate; -- updated present state with next state
end if;
end process stateff;
```

BR 1/99

11

FSM Architecture, Two processes (cont)

```
comblgic:process (zero, cnt_eq, pstate)
begin
-- default assignments
nstate <= pstate;
set_busy <= '0'; clr_busy <= '0';
ld_cnt <= '0';
addr_sel <= '0';
zero_we <= '0';
cnt_en <= '0';
CASE pstate IS
WHEN S0 => if (zero = '1') then
set_busy <= '1'; nstate <= S1;
end if;
WHEN S1 => ld_cnt <= '1'; nstate <= S2;
WHEN S2 => zero_we <= '1'; cnt_en <= '1'; addr_sel <= '1';
if (cnt_eq = '1') then
clr_busy <= '1'; nstate <= S0;
end if;
WHEN others => nstate <= S0;
end case;
end if;
end process comblgic;
```

end a;


BR 1/99

12

Comments on Two Process Implementation

- *Stateff* process defines only FFs
- *Comblogic* process defines
 - State transitions
 - Output assertions
 - Has natural mapping from ASM chart to CASE statement
- Default assignments to outputs in *Comblogic* process very important
 - A combinational process; do not want latches synthesized on outputs
 - The assignment “pstate <= nstate” says to not change state unless directed to from within CASE statement.


FSM Timing: Start Zero Operation

 

Comments

- Note that Pstate changes on active clock edge
- Conditional outputs will change based on present state AND external inputs
- Unconditional outputs change on clock edge and remain true as long as in the current state
- In order for BUSY to go high in State S1, ‘set_busy’ must be asserted in S0 since BUSY comes from JK FF.

FSM Timing: Finish Zero Operation

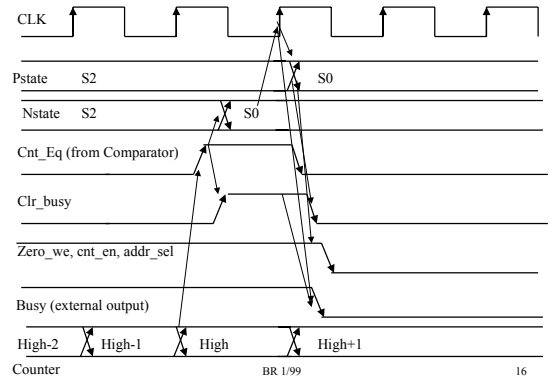

Comments

- Note that for BUSY to go low in S0, then “clr_busy” had to be asserted in State S2.
- Note that the ‘cnt_en’ signal stays true for one clock edge after ‘cnt_eq’ goes true
 - This means that the COUNTER will increment to HIGH+1, sometimes this makes a difference, need to be aware of it