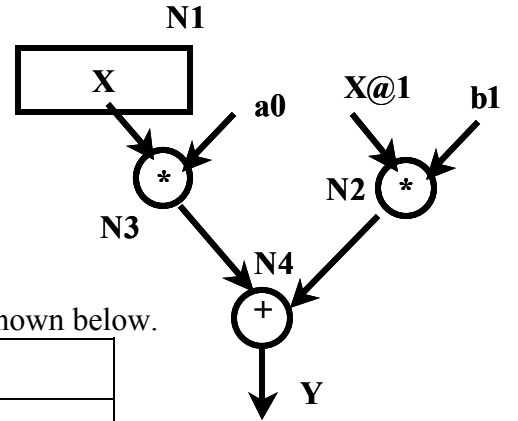



1. Create a schedule for the flowgraph above that increases the initiation rate to its maximum value. Draw the datapath for this scheule


Figure 1



The schedule for initiation rate = 1, latency = 3 and datapath is shown below.

	Sample A	Sample B	Sample C
Clk N	N1(\leftarrow)		
Clk N+1	N2(*), N3(*)	N1(\leftarrow)	
Clk N+2	N4(+)	N2(*), N3(*)	N1(\leftarrow)
Clk N+3		N4(+)	N2(*), N3(*)
Clk N+4			N4(+)

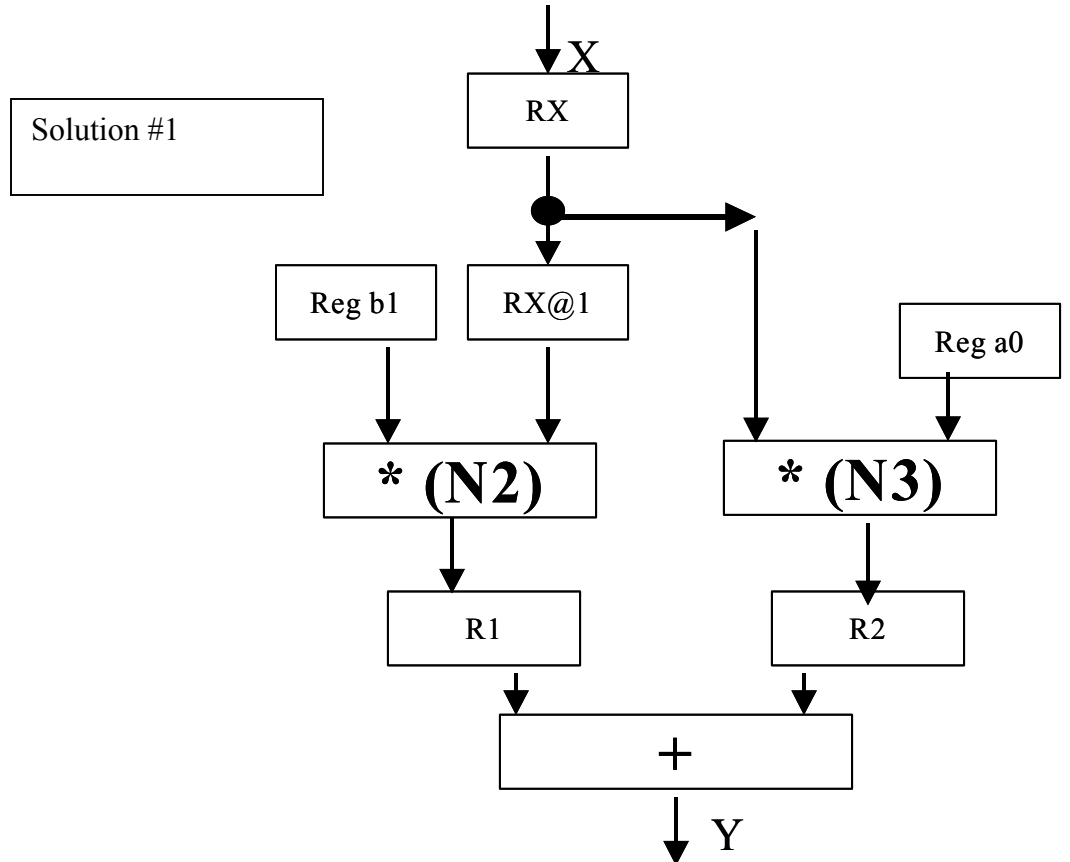

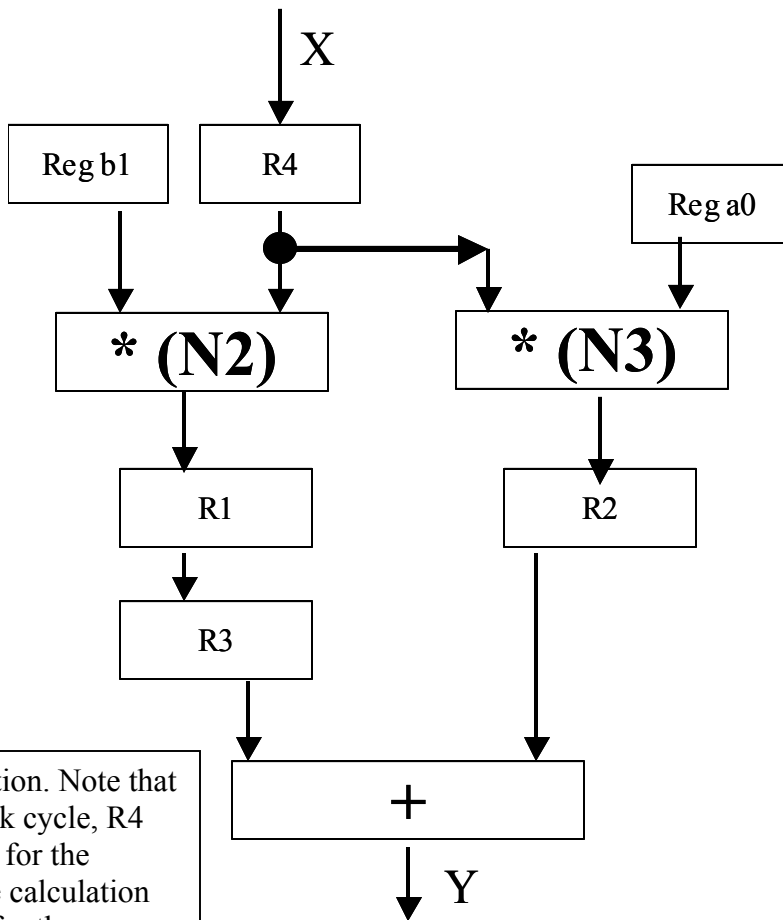

Alternate solution. Note that any given clock cycle, $R4$ contains the X for the current sample calculation and the $X@1$ for the previous sample period. The extra register in the lefthand path delays the $X@1 * b$ calculation by 1 clock period to align with the $X*a0$ calculation.

3. For the flowgraph below, design a schedule and datapath that will achieve the fastest initiation rate.

The value 'Y@1' is the value of the previous computation. (Hint – the fastest initiation rate is 2 --- why???? – you determine the latency)

	Sample J	Sample J+1
Clk 1	N1	
Clk 2	N3, N2 (depends on N4 Sample J-1)	
Clk 3	N4	N1,
Clk 4		N3, N2 (depends on N4 sample J)
Clk 5		N4
Clk 6		

Figure 2

