

Carry look-ahead adder →

The ripple-carry adder, its limiting factor is the time it takes to propagate the carry. The carry look-ahead adder solves this problem by calculating the carry signals in advance, based on the input signals. The result is a reduced carry propagation time.

To be able to understand how the carry look-ahead adder works, we have to manipulate the Boolean expression dealing with the full adder. The Propagate P and generate G in a full-adder, is given as:

$$\begin{array}{ll} P_i = A_i \oplus B_i & \text{Carry propagate} \\ G_i = A_i B_i & \text{Carry generate} \end{array}$$

Notice that both propagate and generate signals depend only on the input bits and thus will be valid after one gate delay.

The new expressions for the output sum and the carryout are given by:

$$\begin{array}{l} S_i = P_i \oplus C_{i-1} \\ C_{i+1} = G_i + P_i C_i \end{array}$$

These equations show that a carry signal will be generated in two cases:

- 1) if both bits A_i and B_i are 1
- 2) if either A_i or B_i is 1 and the carry-in C_i is 1.

Let's apply these equations for a 4-bit adder:

$$\begin{array}{l} C_1 = G_0 + P_0 C_0 \\ C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0 \\ C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \\ C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{array}$$

These expressions show that C_2 , C_3 and C_4 do not depend on its previous carry-in. Therefore C_4 does not need to wait for C_3 to propagate. As soon as C_0 is computed, C_4 can reach steady state. The same is also true for C_2 and C_3

The general expression is

$$C_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_2 P_1 G_0 + P_i P_{i-1} \dots P_1 P_0 C_0.$$

This is a two level circuit. In CMOS however the delay of the function is nonlinearly dependent on its fan in. Therefore large fanin gates are not practical.

Carry look-ahead adder's structure can be divided into three parts: the propagate/generate generator Fig. 1, the sum generator Fig. 2 and the carry generator Fig. 3.

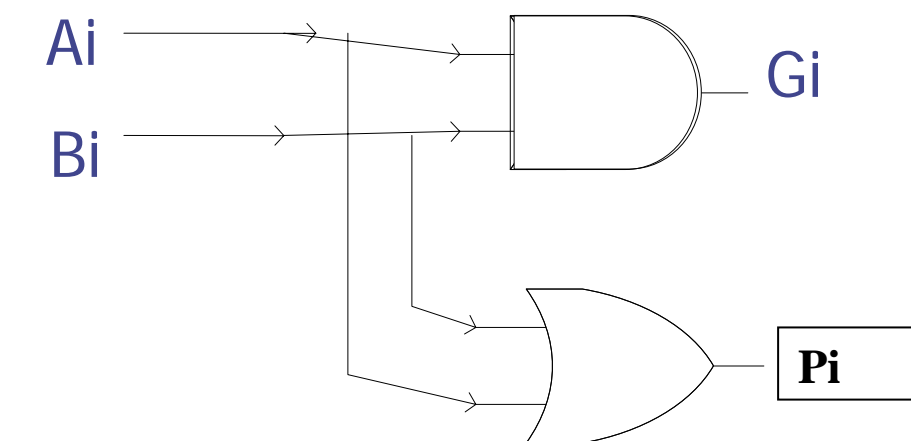


Fig. 1 Propagate /Generate generator

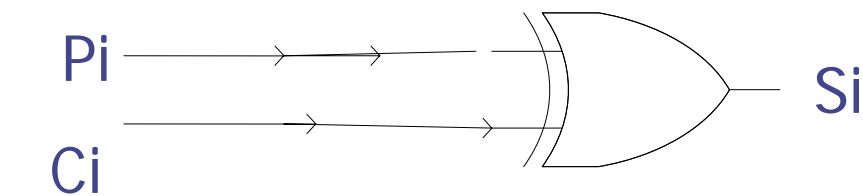


Figure 2: Sum Generator

Figure 4 shows the carry generator needed to add four bits numbers. To make the carry generator from 4 bits to n bits, we need only add AND gates and inputs for the OR gate. The largest AND gate in the carry section has always n+1 inputs and the number of AND gates requirements is n. Therefore the design of a 16 bits adder needs the last carry generator section to have 16 AND gates, where the biggest AND gate has 17 inputs. Also the OR gate in this section needs 17 inputs.

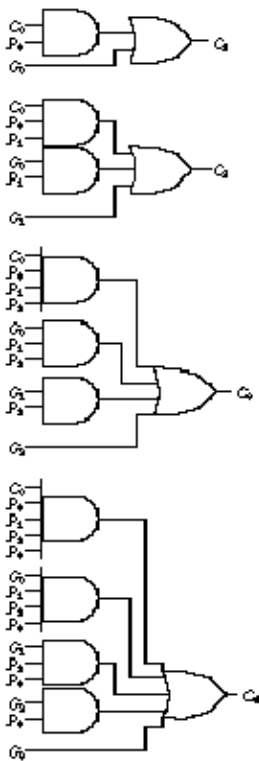


Fig. 3 Look-Ahead Carry generator

The size and fan-in of the gates needed to implement the Carry-Look-ahead adder is usually limited to four, so 4-bit Carry-Look ahead adder is designed as a block. The 4-bit Carry Look Ahead adder block diagram is shown in Fig.4. The delay of such circuit is 4 levels of logic.

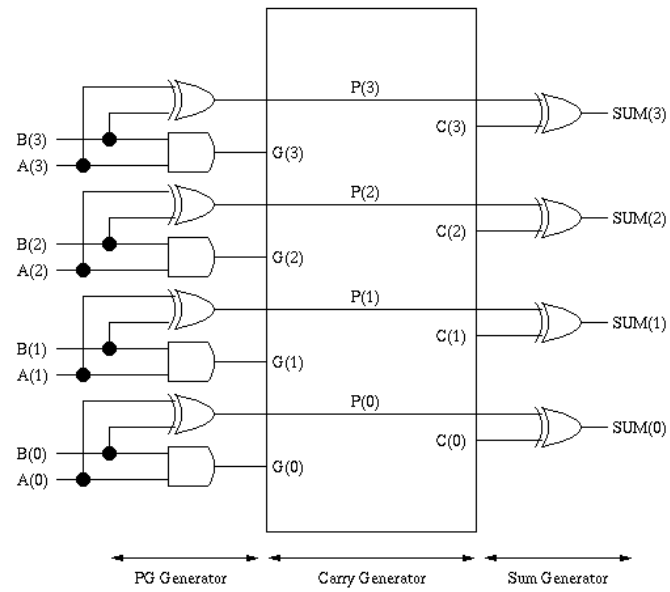


Fig. 1 + Fig. 2 + Fig. 3

Figure 4: 4-bit Carry Look Ahead Adder